


# Decoder, Encoder and Multiplexer

## Multiplexer


A multiplexer has

- $2^n$  data inputs
- $n$  control inputs
- 1 output

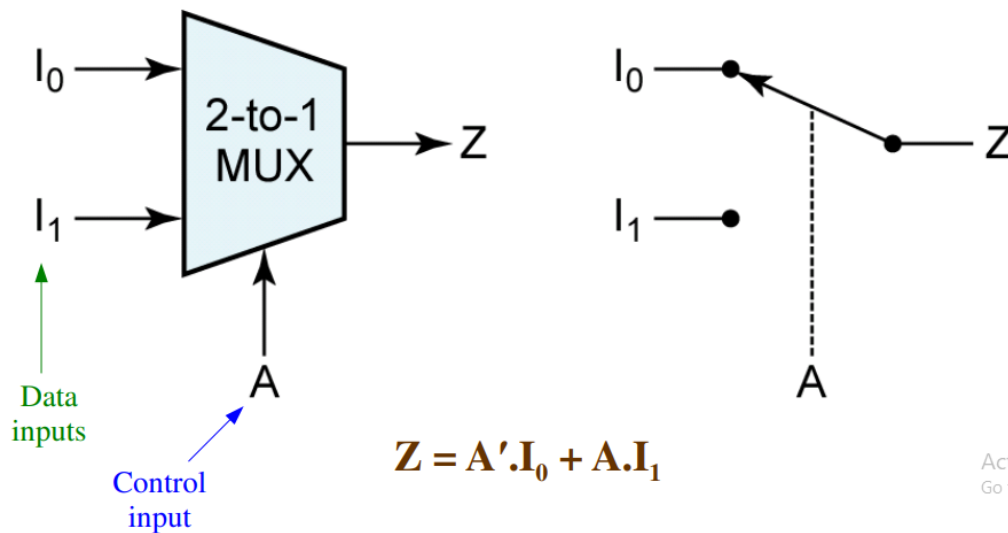A multiplexer routes (or connects) the selected data input to the output. The value of the control inputs determines the data input that is selected.



## Multiplexer in Proteus(74HC157)

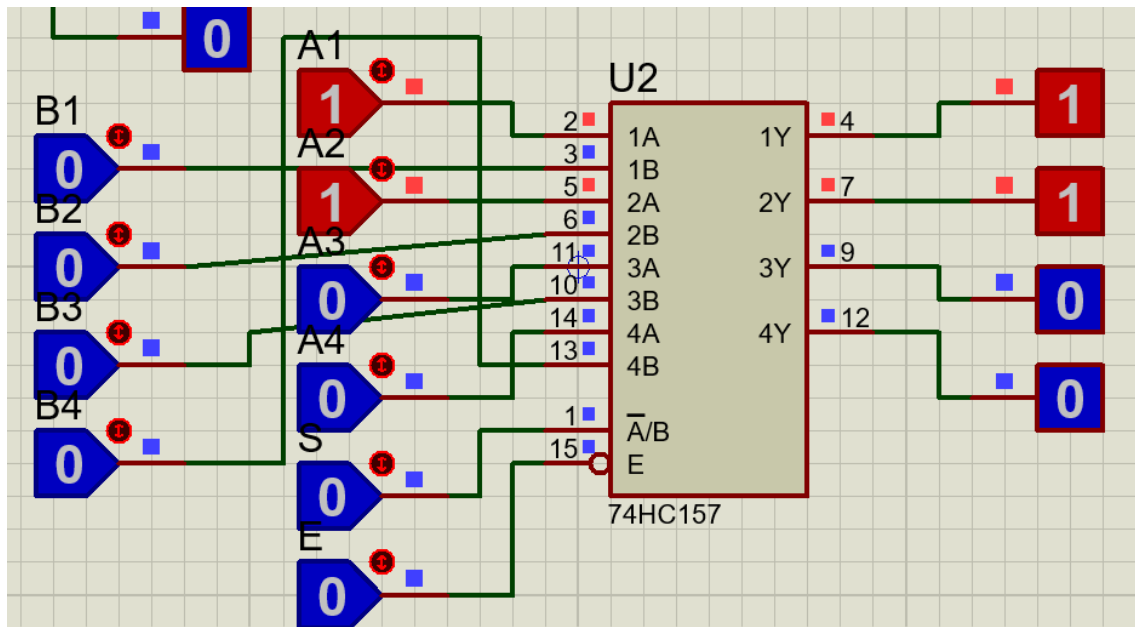


### Decoder

A decoder has


- $n$  inputs
- $2^n$  outputs

A decoder selects one of  $2^n$  outputs by decoding the binary value on the  $n$  inputs.

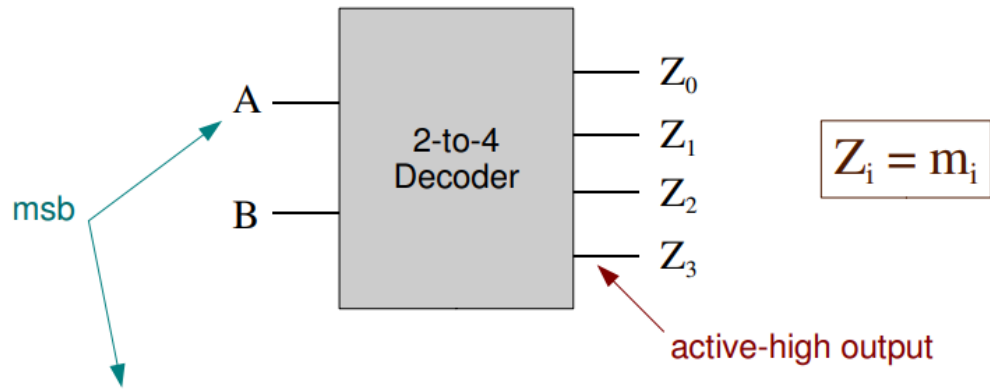The decoder generates all the minterms of the  $n$  input variables. Exactly one output will be active for each combination of the inputs.




| A | B | $Z_0$ | $Z_1$ | $Z_2$ | $Z_3$ |       |
|---|---|-------|-------|-------|-------|-------|
| 0 | 0 | 1     | 0     | 0     | 0     | $m_0$ |
| 0 | 1 | 0     | 1     | 0     | 0     | $m_1$ |
| 1 | 0 | 0     | 0     | 1     | 0     | $m_2$ |
| 1 | 1 | 0     | 0     | 0     | 1     | $m_3$ |

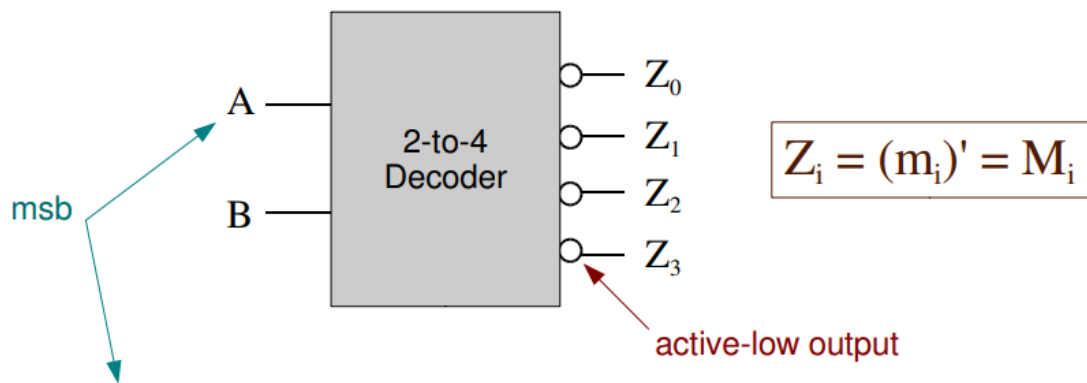

| A | B | $Z_0$ | $Z_1$ | $Z_2$ | $Z_3$ |       |
|---|---|-------|-------|-------|-------|-------|
| 0 | 0 | 0     | 1     | 1     | 1     | $M_0$ |
| 0 | 1 | 1     | 0     | 1     | 1     | $M_1$ |
| 1 | 0 | 1     | 1     | 0     | 1     | $M_2$ |
| 1 | 1 | 1     | 1     | 1     | 0     | $M_3$ |

## Decoder in Proteus (74HC139)

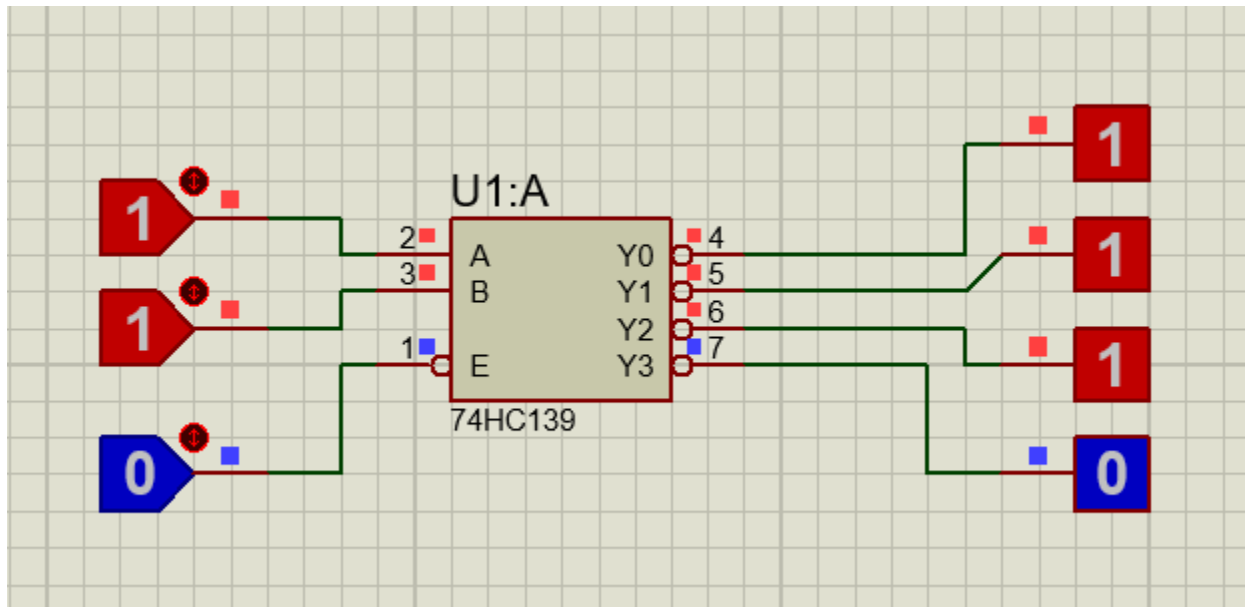


## Encoder

An encoder has

- $2^n$  inputs
- $n$  outputs

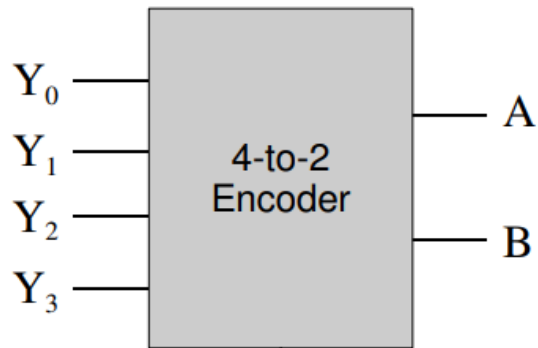Outputs the binary value of the selected (or active) input. Performs the inverse operation of a decoder.



| $Y_0$ | $Y_1$ | $Y_2$ | $Y_3$ | A | B |
|-------|-------|-------|-------|---|---|
| 1     | 0     | 0     | 0     | 0 | 0 |
| 0     | 1     | 0     | 0     | 0 | 1 |
| 0     | 0     | 1     | 0     | 1 | 0 |
| 0     | 0     | 0     | 1     | 1 | 1 |

### Encoder in proteus (4532)

